

Self-Biased Sub-1V Bandgap Reference Circuit

Under supervision of:

Dr. Hesham Omran
TA. Moatasem bayoumy
TA. Ahmed Muhammed

Specs required for the band gap reference circuit:

Technology	65nm
Supply voltage	2
Corners	Temp: -40 to 125 Process: SS, SF, FS, FF
Output voltage	0.8
Bias current	< 10uA
Phase margin	> 60°

BGR core circuit:

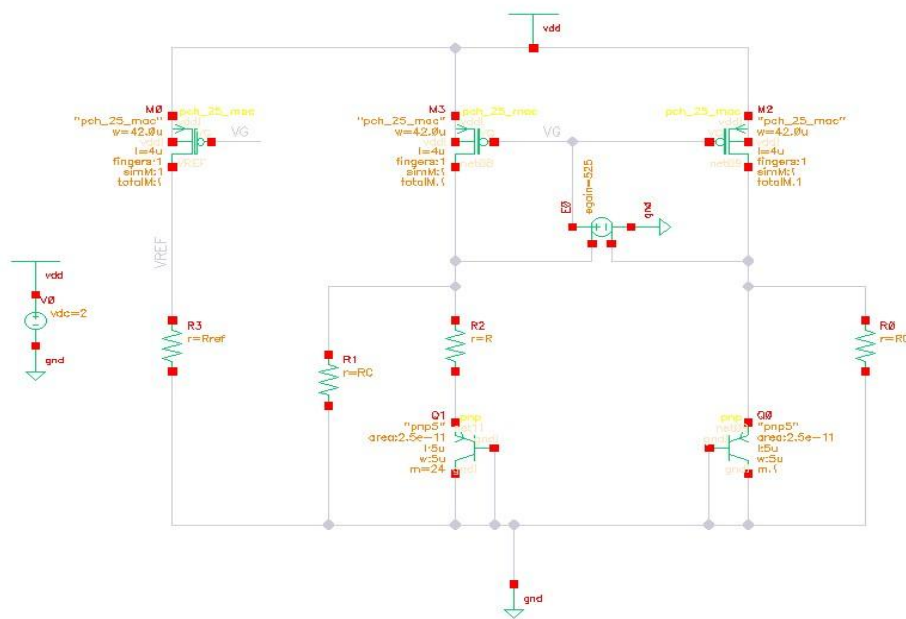


Figure 1 Schematics with device sizing

Hand analysis of the core circuit:

- After getting the characteristics of the BJT:
- Assume current in each branch = 1 μ A

$$V_{BE,Q0} = 660.2 \text{ mV}$$

$$V_{BE,Q1} = 577.3 \text{ mV}$$

$$\Delta V_{BE} = 82.7 \text{ mV}$$

$$\therefore R_2 = \frac{\Delta V_{BE}}{I_{/2}} = 165.4 \text{ kohm}$$

$$R_{1,3} = \frac{V_{BE,Q0}}{I_{/2}} = 1.3204 \text{ Mohm}$$

$$R_{REF} = \frac{V_{REF}}{I} = 800 \text{ kohm}$$

Design of the PMOS devices:

The considerations I took in my design are:

- The inversion level of the devices is weak.
- large length, to avoid mismatch.

DC OP of the core circuit:

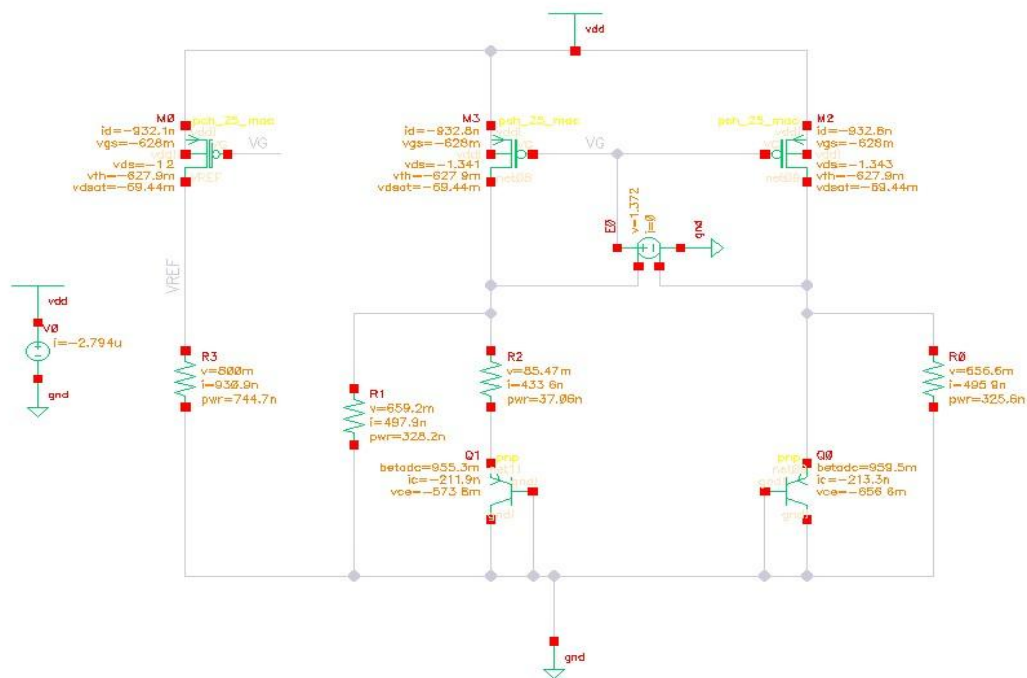


Figure 2 Schematics with DC OP and node voltages annotated

V_{REF} VS temp across nominal corners:

 


Figure 3 Change of reference voltage at nominal corners with temp

V_{ref} vs temperature (-40 to 125) at TT, SS, FF, SF, FS:

 


Figure 4 Change of reference voltage across corners with temp

Band gap reference circuit with actual error amplifier:

The consideration I took in designing the error amplifier:

- We need a high gain around 500.
- Current consumption in the OTA does not exceed 1 μA
- We designed the OTA so that its input pair has low V_{GS} , which means the device will be in the deep subthreshold region, so that the tail current source has a V_{dsat} margin and kept in saturation.

 


Figure 5 Schematics of the error amplifier with device sizing

 


Figure 6 Schematics of whole circuit with device sizing

DC OP of core circuit and error amplifier:

 


Figure 7 DC OP of the error amplifier

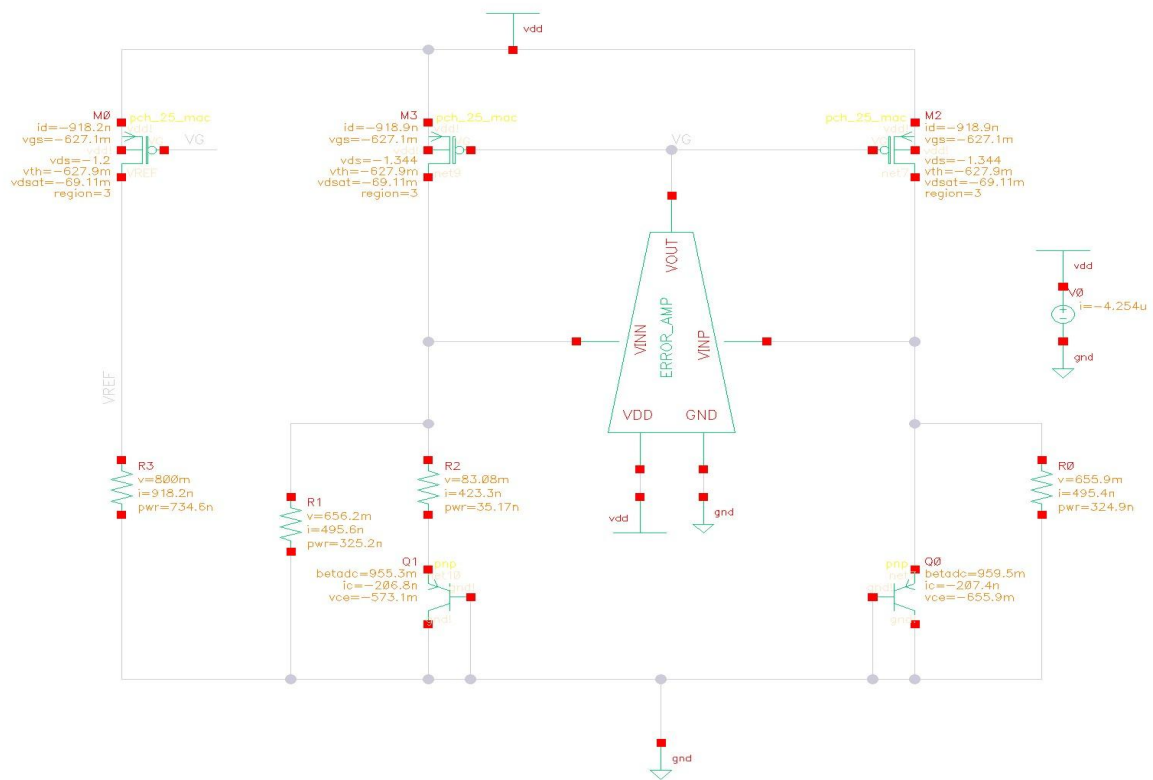


Figure 8 DC OP of the core circuit with actual error amplifier

V_{REF} VS temp across nominal corners:

 


Figure 9 Change of reference voltage at nominal corners with temp

V_{ref} vs temperature (-40 to 125) at TT, SS, FF, SF, FS:

 


Figure 10 Change of reference voltage across corners with temp

STB analysis results:

 


Figure 11 DC loop gain of the error amplifier

 


Figure 12 phase margin and unity gain frequency

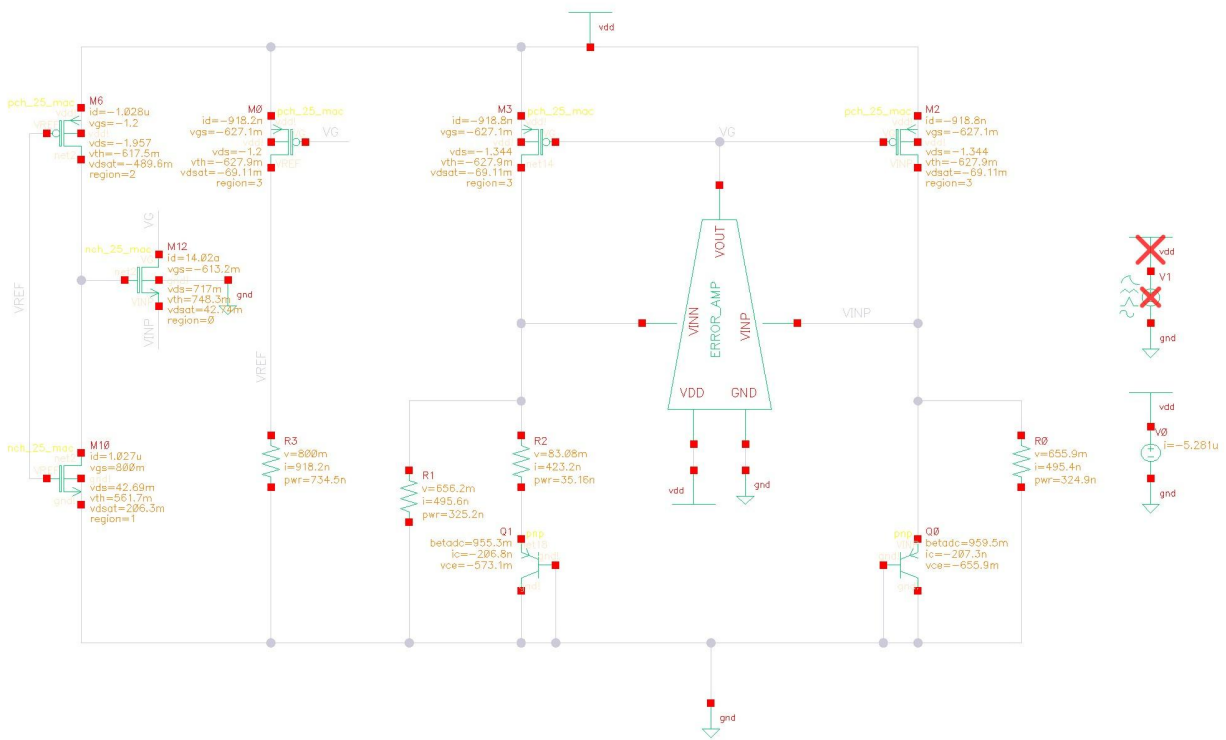


Figure 15 DC OP of the circuit with the start up circuit

 


Figure 16 DC OP of the error amplifier

Transient simulation of V_{REF} as a ramp from (0,0) to (1ms,2V):

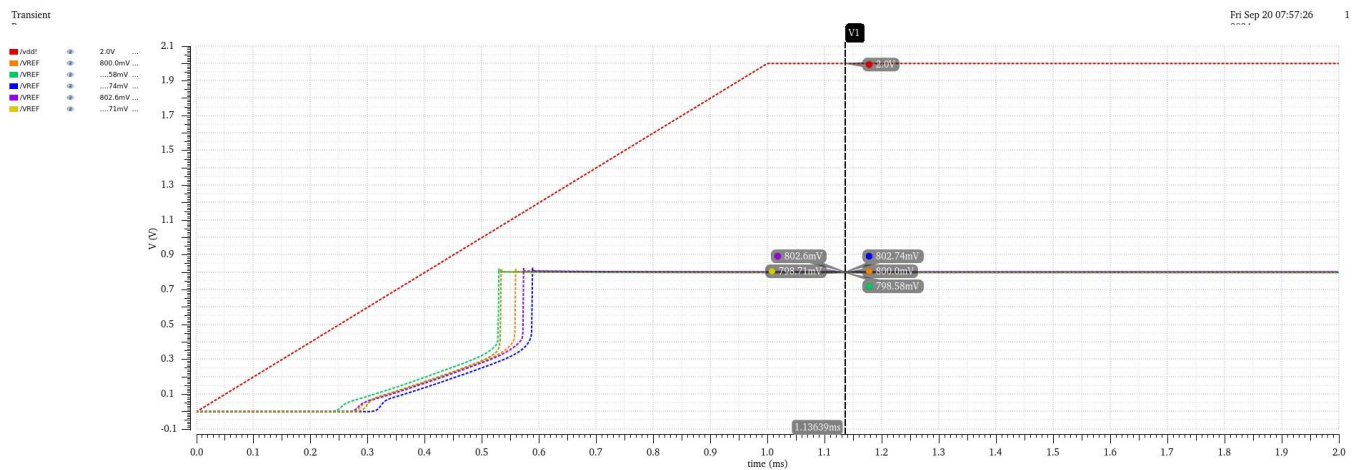


Figure 17 V_{DD} as a ramp and V_{REF} across corners

From these results, all specs are achieved:

- Spec of phase margin has been achieved: 62 deg
- Spec of power consumption has been achieved: 5.28 μ A
- Spec of V_{REF} has been achieved: 800 mV